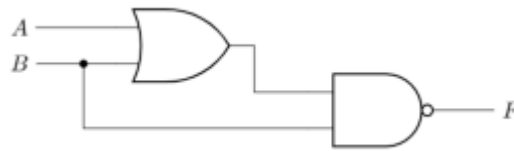



## Boolean 0

- Find Boolean expressions that are equivalent to the following logic diagrams. DO NOT SIMPLIFY!


a.  $F = \overline{(A + B) \times B}$



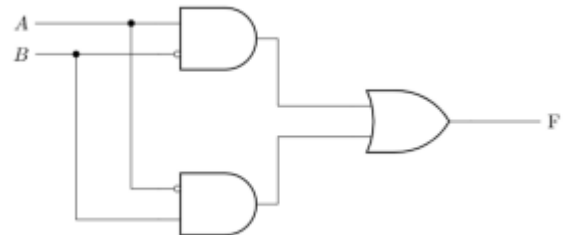b.  $F = (A \times \bar{B}) + (\bar{A} \times B)$




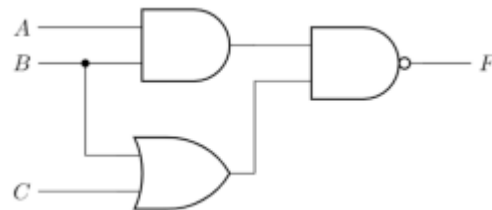c.  $F = \overline{(A \times B) \times (B + C)}$




- Draw logic circuits that are equivalent to the following Boolean expressions. DO NOT SIMPLIFY!


a.  $\overline{(A + B)} + (A + B)$

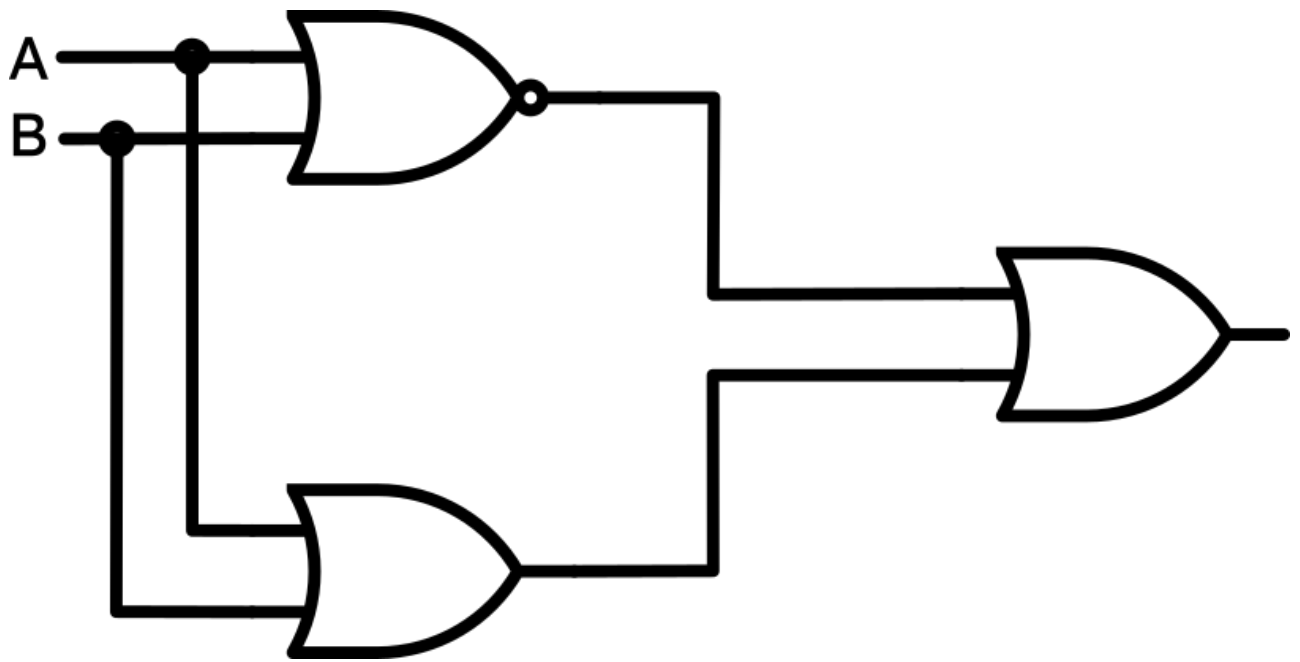

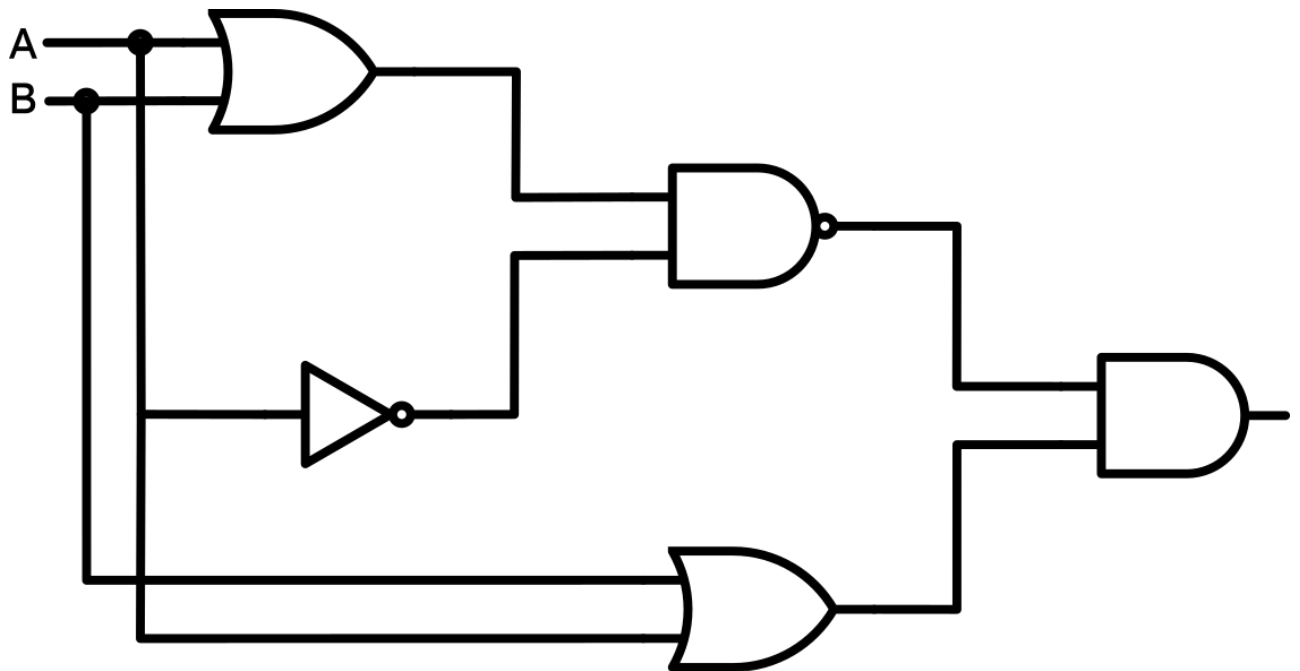b.  $\overline{(A + B) \times \bar{A} \times (B + A)}$



3. For the following logic circuit:

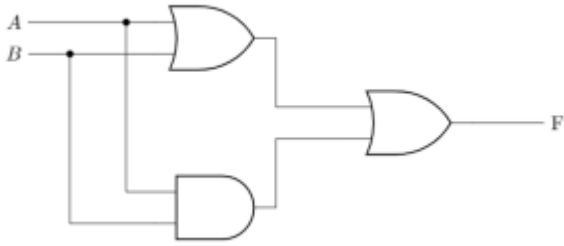


a. Find an equivalent Boolean expression

- $(A + B) + (A \times B) = F$

b. Reduce the expression to its simplest form

- $(A + B) + (A \times B) =$
- $((A + B) + A) \times ((A + B) + B) =$
- $(A + B) \times (A + B) =$
- $(A + B)$

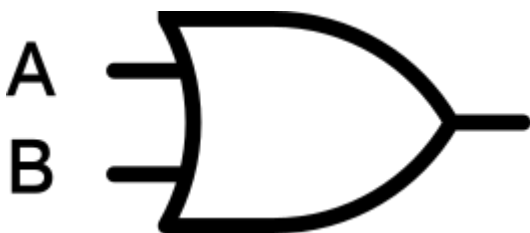c. Convert the simple expression into a logic circuit that is equivalent to the original circuit.



4. Complete the truth table to show that  $\overline{(A \times B)} = \bar{A} + \bar{B}$

<b>A</b>	<b>B</b>	<b>(A × B)</b>	<b><math>\overline{(A \times B)}</math></b>	<b><math>\bar{A}</math></b>	<b><math>\bar{B}</math></b>	<b><math>\bar{A} + \bar{B}</math></b>
1	1	1	0	0	0	0
1	0	0	1	0	1	1
0	1	0	1	1	0	1
0	0	0	1	1	1	1